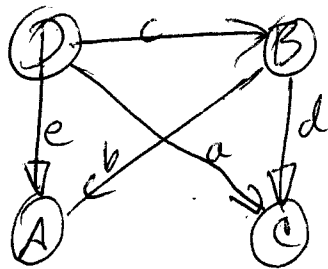


# MATH 410 (BAYLY) SELECTED SOLUTIONS ①

2.6.5



I'll let you do the calculations!

(a)

$$A = \begin{matrix} & \begin{matrix} A & B & C & D \end{matrix} \\ \begin{matrix} a \\ b \\ c \\ d \\ e \end{matrix} & \begin{pmatrix} 0 & 0 & 1 & -1 \\ 1 & -1 & 0 & 0 \\ 0 & 1 & 0 & -1 \\ 0 & -1 & 1 & 0 \\ 1 & 0 & 0 & -1 \end{pmatrix} \end{matrix}$$

(b) RANK = 3

(c)  $\dim \text{RANGE}(A) = \text{rank} = 3 = \dim \text{COKERNEL}(A)$

$\dim \text{KERNEL}(A) = n - r = 4 - 3 = 1$

$\dim \text{COKERNEL}(A) = m - r = 5 - 3 = 2$

(d) Basis for KERNEL is  $\left\{ \begin{pmatrix} 1 \\ -1 \\ 0 \\ 0 \\ 0 \end{pmatrix} \right\}$

★ see problem 2.6.11

We know from 2.6.11

that this vector is ALWAYS a kernel vector, and is the ONLY kernel vector if the graph is IN ONE PIECE

Basis for COKERNEL consists of the INDEPENDENT LOOPS.

(2)

The loop  $A \rightarrow B \rightarrow D$  can be written as the

$$\text{vector } \begin{matrix} d \\ b \\ c \\ d \\ e \end{matrix} \begin{pmatrix} 0 \\ -1 \\ -1 \\ 0 \\ +1 \end{pmatrix} \leftarrow \vec{s}_1$$

These TWO vectors SPAN the KERNEL

The loop  $B \rightarrow C \rightarrow D$  can be written by the vector

$$\begin{matrix} a \\ b \\ c \\ d \\ e \end{matrix} \begin{pmatrix} -1 \\ 0 \\ 1 \\ 1 \\ 0 \end{pmatrix} = \vec{s}_2 \text{ the cokernel of } A$$

(c) The SOLVABILITY CONDITION for  $A\vec{x} = \vec{b}$  is for  $\vec{s}_1^T \vec{b} = 0$ ,  $\vec{s}_2^T \vec{b} = 0$

(f) Explicitly, if  $\vec{b} = \begin{pmatrix} \alpha \\ \beta \\ \gamma \\ \delta \\ \epsilon \end{pmatrix}$ , we need

$$\vec{s}_1^T \vec{b} = -\beta - \gamma + \epsilon = 0 \quad \text{i.e. } \epsilon = \beta + \gamma$$

$$\vec{s}_2^T \vec{b} = -\alpha + \gamma + \delta = 0 \quad \text{i.e. } \delta = \alpha - \gamma$$

SO any  $\begin{pmatrix} \alpha \\ \beta \\ \gamma \\ \alpha - \gamma \\ \beta + \gamma \end{pmatrix}$  will work!  $\begin{pmatrix} 1 \\ 2 \\ 3 \\ -2 \\ 5 \end{pmatrix}$  for example.

(3)

Row-reduction (with swaps)

$$\left( \begin{array}{cccc|c} 0 & 0 & 1 & -1 & 1 \\ 1 & -1 & 0 & 0 & 2 \\ 0 & 1 & 0 & -1 & 3 \\ 0 & -1 & 1 & 0 & -2 \\ 1 & 0 & 0 & -1 & 5 \end{array} \right) \rightarrow \left( \begin{array}{cccc|c} x & y & z & w & \\ 1 & -1 & 0 & 0 & 2 \\ 0 & 1 & 0 & -1 & 3 \\ 0 & 0 & 1 & -1 & 1 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{array} \right) \begin{array}{l} \leftarrow \text{OK!} \\ \leftarrow \text{OK!} \end{array}$$

$(A|b)$   $U | \vec{c}$

$$\Rightarrow z = w + 1 \quad y = w + 3 \quad x = w + 5$$


General solution  $\vec{x} = \begin{pmatrix} 5 \\ 3 \\ 1 \\ 0 \end{pmatrix} + w \begin{pmatrix} 1 \\ -1 \\ 0 \\ -1 \end{pmatrix}$

# 6.2.2 (sketch solution)

4

Let's use A, B, C, D for nodes ~~A, B, C, D~~  
 as in 2.6.5, edges a, b, c, d, e

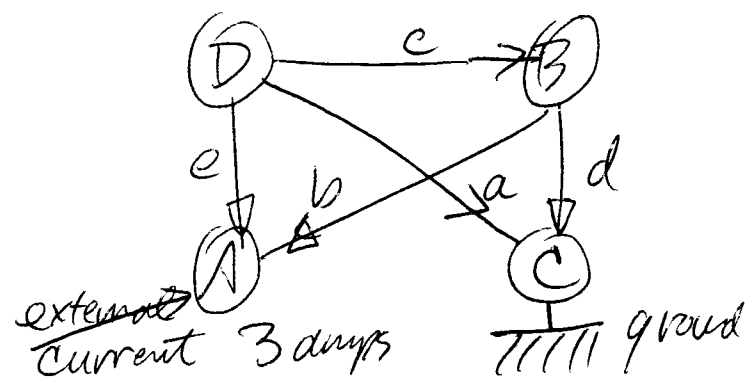so that  $A = \begin{pmatrix} 0 & 0 & -1 & 1 \\ 1 & -1 & 0 & 0 \\ 0 & 1 & 0 & -1 \\ 0 & -1 & 1 & 0 \\ 1 & 0 & 0 & -1 \end{pmatrix}$



If  $\vec{V} = \begin{pmatrix} V_A \\ V_B \\ V_C \\ V_D \end{pmatrix}$  is the vector of voltages (to be solved for)

then the vector of currents is

$$\vec{I} = \begin{pmatrix} I_a \\ I_b \\ I_c \\ I_d \\ I_e \end{pmatrix} = R^{-1} A \vec{V} = A \vec{V} \text{ since all resistances are } 1 \text{ OHM}$$

KIRCHOFF'S CURRENT LAW says  $A^T \vec{I} = \vec{0}$  for the internal nodes, which are B & D.

So we just use the rows of  $A^T$  that correspond to nodes B & D, which are

	a	b	c	d	e	
A	0	1	0	0	1	row A
B	0	-1	1	-1	0	row B
C	-1	0	0	1	0	
D	1	0	-1	0	-1	row D

KIRCHHOFF'S CURRENT LAW also applies to node A where the external current 3 amps must be canceled by total NEGATIVE current of 3 amps along edges b, e

FOR THIS WE USE ROW A of AT

AT node C, current is allowed to escape to ground so no KCL. But being ground means  $V_C = 0$

So we have

$$\left. \begin{aligned} (0 \ 1 \ 0 \ 0 \ 1) \vec{AV} &= -3 \\ (0 \ -1 \ 1 \ -1 \ 0) \vec{AV} &= 0 \\ (-1 \ 0 \ -1 \ 0 \ -1) \vec{AV} &= 0 \end{aligned} \right\} \begin{array}{l} 4 \text{ equations} \\ \text{for } \vec{V} \end{array}$$


and  $V_C = 0$

ILP.

$$\begin{pmatrix} 2 & -1 & 0 & -1 \\ -1 & 3 & -1 & -1 \\ -1 & -1 & -1 & 3 \\ 0 & 0 & 1 & 0 \end{pmatrix} \begin{pmatrix} V_A \\ V_B \\ V_C \\ V_D \end{pmatrix} = \begin{pmatrix} -3 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

This you can solve!
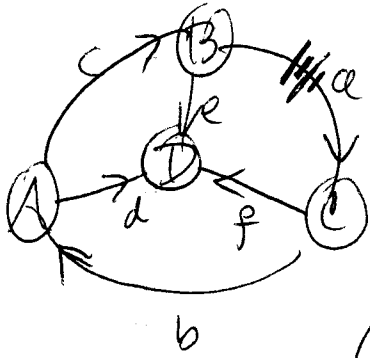
### 6.2.6 Beginning only! It's easier to draw



Each edge has a  $3\Omega$  resistor;  
edge a has a 10 volt battery.

They want us to find current  $I_d$   
(as well as all other currents for me!)

There are NO grounds or external nodes; ONLY  
the battery adds 10 volts ~~to~~ ~~subtract~~ ~~from~~  ~~$I_a R_a$~~

so that  $I_a = R_a^{-1} (V_C - V_D + 10)$

[I am probably ~~making~~ <sup>violating</sup> ANOTHER  $\pm$  sign convention!]

Everything stays the same, now:  $A^T \vec{I} = \vec{0}$  at every node

$$\Rightarrow A^T R^{-1} A \vec{V} = -A^T \begin{pmatrix} R_a^{-1} 10 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

This simplifies since all R's are = 3, so

$$\begin{pmatrix} 3 & -1 & -1 & -1 \\ -1 & 3 & -1 & -1 \\ -1 & -1 & 3 & -1 \\ -1 & -1 & -1 & 3 \end{pmatrix} \begin{pmatrix} V_A \\ V_B \\ V_C \\ V_D \end{pmatrix} = \begin{pmatrix} 0 \\ 10 \\ -10 \\ 0 \end{pmatrix}$$

which you can  
now go ahead  
and solve!